


2.9

4.0

24 V DC +

24 V DC +

Q3.1

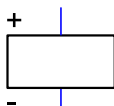

2.9

4.0


24 V DC -

F

O

$$\begin{array}{r} 1.3 \\ 1.3 \\ 1.3 \end{array}$$

Q3.5

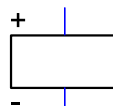

F

o

1.5
1.5
1.5

24 V DC -

Schema Beispiel
Exemple de schéma
Esempio di schema

USIE / SwissSkills Zurich 2016


CS-2016_Exemple de schéma-Feuille-03.DWG



Date 08.11.2016

Créé VSEI / cf

Blatt
Feuille
Foglio
03

	0	1	2	3	4	5	6	7	8	9	
A	<div>3.9</div> <div>24 V DC +</div> <div></div> <div></div> <div></div> <div></div> <div></div> <div></div> <div></div> <div></div> <div>5.0</div> <div>24 V DC +</div>										A
B											B
C											C
D	<div>3.9</div> <div>24 V DC -</div> <div></div> <div></div> <div></div> <div></div> <div></div> <div></div> <div></div> <div></div> <div>5.0</div> <div>24 V DC -</div>										D
E											E
F	<div>Schema Beispiel</div> <div>Exemple de schéma</div> <div>Esempio di schema</div> <div>USIE / SwissSkills Zurich 2016</div> <div>CS-2016_Exemple de schéma-Feuille-04.DWG</div> <div><div>Championnat suisse de la branche électrique ZÜRICH 2016 du 22 au 26 novembre Messe Zürich</div></div> <div><div>Date</div>08.11.2016</div> <div><div>Créé</div>VSEI / cf</div> <div>Blatt Feuille Foglio 04</div>										F
	0	1	2	3	4	5	6	7	8	9	

